

(A)

NAME:

NEPTUN:

MEASURE AND DATA PROCESSING EXAM

28.11.2023


1. The table gives the current and voltage of a resistor. Find the value of the resistor and complete the table! Calculation required!

I [mA]	1.27	2.98	4.04	4.68
U [V]				22

2. Complete the table!


Sign	U	I	R	C	t	Q
Unit	V					

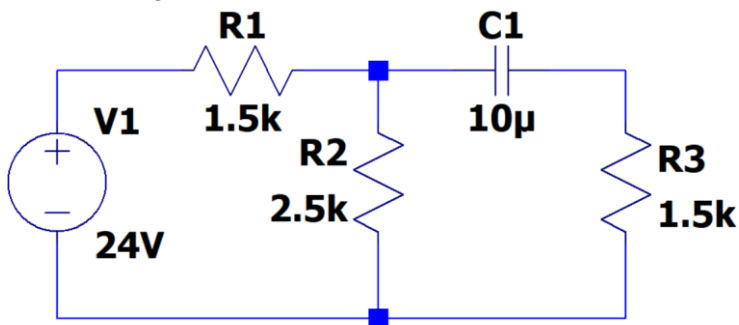3. Calculate the voltage and current of all the resistors, after the transient of the circuit. Only the values are not enough!




UR1=
IR1=
UR2=
IR2=
UR3=
IR3=

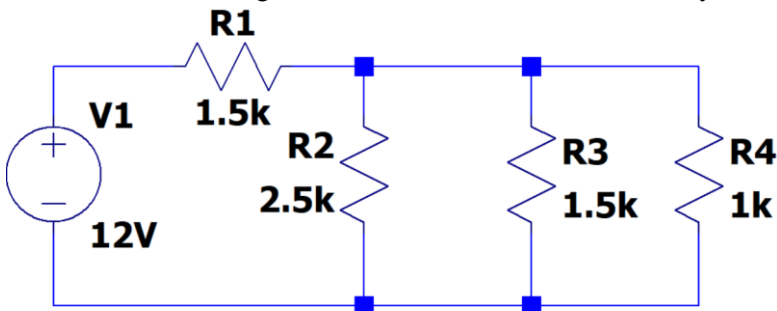4. Calculate the voltage and current of all the resistors. Only the values are not enough!



UR1=
IR1=
UR2=
IR2=
UR3=
IR3=
UR4=
IR4=

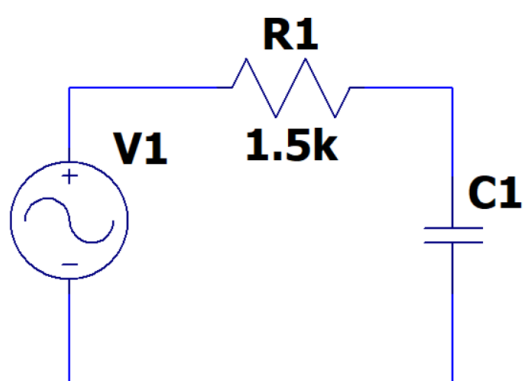5. What value of capacitor is needed in the following circuit to have a time constant of 150 μ s?



C=

(B)

NAME:

NEPTUN:

MEASURE AND DATA PROCESSING EXAM

28.11.2023


1. The table gives the current and voltage of a resistor. Find the value of the resistor and complete the table! Calculation required!

U [V]	4	10	12	19
I [mA]	5.88			

2. Complete the table!


Sign	U	Q	R	I	t	C
Unit	V					

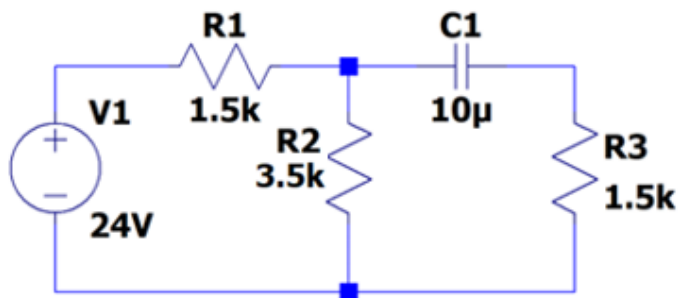3. Calculate the voltage and current of all the resistors, after the transient of the circuit. Only the values are not enough!




UR1=
IR1=
UR2=
IR2=
UR3=
IR3=

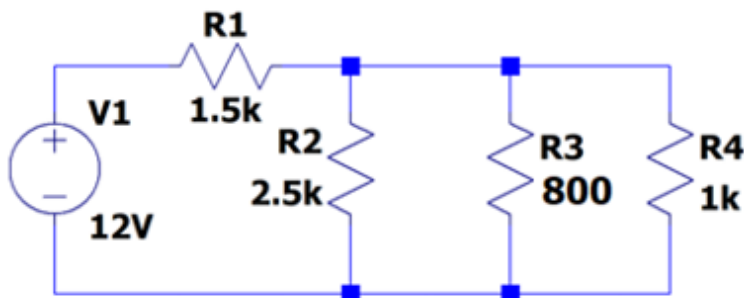4. Calculate the voltage and current of all the resistors. Only the values are not enough!



UR1=
IR1=
UR2=
IR2=
UR3=
IR3=
UR4=
IR4=

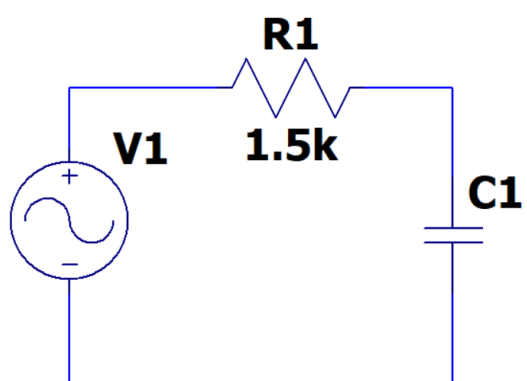5. What value of capacitor is needed in the following circuit to have a time constant of 100 μ s?



C=

$$B) I = U/R = 4V/5.88 \text{ mA} \approx 680 \Omega$$

$$1,$$

$U [V]$	4	10	12	19
$I [\text{mA}]$	5.88	14.7	17.64	22.94

$$2,$$

U	R	R	I	t	C
V	C/As	Ω	A	s	F

$$3, \quad U_{R3} = I_{R3} = \text{because of } C1$$

$$R_{\text{sum}} = R_1 + R_2 = 1,5k\Omega + 3,5k\Omega = 5k\Omega$$

$$I_{\text{sum}} = U/R_{\text{sum}} = 24V/5k\Omega = \underline{4,8 \text{ mA}} = I_{R1} = I_{R2}$$

$$U_{R1} = I_{\text{sum}} \cdot R_1 = \underline{7,2V}$$

$$U_{R2} = I_{\text{sum}} \cdot R_2 = \underline{16,8V}$$

$$4, \quad R_{\text{sum}} = (R_2 \times R_3 \times R_4) + R_1 = 377\Omega + 15k\Omega = \underline{1877\Omega}$$

$$I_{\text{sum}} = U/R_{\text{sum}} = 12V/1877\Omega = \underline{6,39 \text{ mA}} = I_{R1}$$

$$U_{R1} = I_{\text{sum}} \cdot R_1 = 6,39 \text{ mA} \cdot 1,5k = \underline{9,58V}$$

$$U_{R2} = U_{R3} = U_{R4} = U - U_{R1} = 12V - 9,58V = \underline{2,42V}$$

$$I_{R2} = U/R_2 = 2,42V/2,5k = \underline{0,968 \text{ mA}}$$

$$I_{R3} = U/R_3 = 2,42V/98k = \underline{0,025 \text{ mA}}$$

$$I_{R4} = U/R_4 = 2,42V/1k = \underline{2,42 \text{ mA}}$$

$$5, \quad T = RC \Rightarrow C = \frac{T}{R} = \frac{100\mu s}{1,5k\Omega} = \underline{66,67 \text{ nF}}$$

A) 1. $R = U/I = 22V / 4.68mA = 4.7k\Omega$

$I [mA]$	1.27	2.98	4.04	4.68
$U [V]$	~6	14	~19	22

2,

U	I	R	C	t	Q
V	A	Ω	F	s	C/As

3, $U_{R3} = I_{R3} = \emptyset$, because of CA

$R_{tot} = R_1 + R_2 = 1.5k + 2.5k = 4k\Omega$

$I_c = U/R = 24V / 4k\Omega = 6mA \Rightarrow I_{R1} = I_{R2} = \underline{\underline{6mA}}$

$U_{R1} = I_{tot} \cdot R_1 = 6mA \cdot 1.5k\Omega = \underline{\underline{9V}}$

$U_{R2} = I_{tot} \cdot R_2 = 6mA \cdot 2.5k\Omega = \underline{\underline{15V}}$

4, $R_{tot} = (R_2 \times R_3 \times R_4) + R_1 = 1.5k + 480 \approx 1980\Omega$

$I_{tot} = U / R_{tot} = 12V / 1.98k = \underline{\underline{6.05mA}} = I_{R1}$

$U_{R1} = I_{R1} \cdot R_1 = 6.05mA \cdot 1.5k = \underline{\underline{9.075V}}$

$U_{R2} = U_{R3} = U_{R4} = U - U_{R1} = 12V - 9.075V = \underline{\underline{2.925V}}$

$I_{R2} = U_{R2} / R_2 = 2.925V / 2.5k = \underline{\underline{1.17mA}}$

$I_{R3} = U_{R3} / R_3 = 2.925V / 1.5k = \underline{\underline{1.95mA}}$

$I_{R4} = U_{R4} / R_4 = 2.925V / 1k = \underline{\underline{2.925mA}}$

5, $T = RC \Rightarrow C = \frac{T}{R} = \frac{150ps}{1.5k} = \underline{\underline{100nF}}$