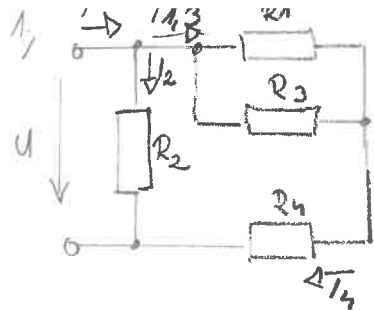




$$\begin{aligned} R_1 &= 60\Omega \\ R_2 &= 200\Omega \\ R_3 &= 30\Omega \\ R_4 &= 180\Omega \\ U &= 24V \end{aligned}$$

$$R_c = \underbrace{((R_1 \times R_3) + R_4)}_{20\Omega} \times R_2 = 100\Omega \Rightarrow I = U/R_c = 24V/100\Omega = \underline{\underline{240mA}}$$

$$U_{R2} = U = 24V$$

$$I_{R2} = U/R_2 = 24V/200\Omega = \underline{\underline{120mA}}$$


$$\begin{aligned} \text{Mittel } \left. \begin{aligned} I_{R3} &= I_4 \\ I_4 + I_{R2} &= I \end{aligned} \right\} \Rightarrow I - I_{R2} &= I_4 = 240mA - 120mA = \underline{\underline{120mA}} \end{aligned}$$

$$U_{R4} = I_4 \cdot R_4 = 120mA \cdot 180\Omega = \underline{\underline{21,6V}}$$

$$\left. \begin{aligned} U_{R1} &= U_{R3} \\ U_{R1} + U_{R4} &= U \end{aligned} \right\} U - U_{R4} = U_{R1} = 24V - 21,6V = \underline{\underline{2,4V}}$$

$$\left. \begin{aligned} I_{R1} &= U_{R1}/R_1 = 2,4V/60\Omega = \underline{\underline{40mA}} \\ I_{R3} &= U_{R3}/R_3 = 2,4V/30\Omega = \underline{\underline{80mA}} \end{aligned} \right\} \Sigma: I_{R1} + I_{R3} = I_4 \quad \checkmark$$

2;

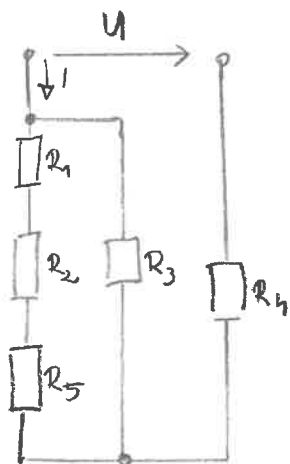

$$\begin{aligned} R_1 &= 20\Omega \\ R_2 &= 91\Omega \\ R_3 &= 75\Omega \\ R_4 &= 10\Omega \\ R_5 &= 30\Omega \\ U &= 120V \end{aligned}$$

$$R_c = \underbrace{((R_1 + R_2 + R_5) \times R_3)}_{150\Omega} + R_4 = 60\Omega$$

$$I = U/R_c = 12V/60\Omega = \underline{\underline{200mA}}$$

$$I_{R4} = I = \underline{\underline{200mA}}$$

$$U_{R4} = I_{R4} \cdot R_4 = 200mA \cdot 10\Omega = \underline{\underline{2V}}$$


$$U_{R3} = U - U_{R4} = 12V - 2V = \underline{\underline{10V}}$$

$$I_{R3} = U_{R3}/R_3 = 10V/75\Omega = \underline{\underline{133mA}}$$

$$I_{R1} = I_{R2} = I_{R5} \Rightarrow I - I_{R3} = 200 \mu A - 130 \mu A = \underline{67 \mu A}$$

$$\left. \begin{aligned} U_{R1} &= I_{R3} \cdot R_3 = 67 \mu A \cdot 20 \Omega = 1,34 V \\ U_{R2} &= I_{R3} \cdot R_2 = 67 \mu A \cdot 0,1 k\Omega = 6,7 V \\ U_{R5} &= I_{R3} \cdot R_5 = 67 \mu A \cdot 30 \Omega = 2,01 V \end{aligned} \right\} \sum U_{R1} + U_{R2} + U_{R5} = U_{R3}$$

3,

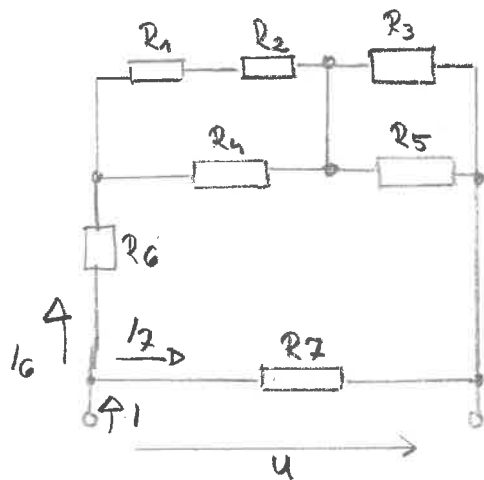

$$\begin{aligned} R_1 &= 2 k\Omega \\ R_2 &= 3 k\Omega \\ R_3 &= 4 k\Omega \\ U &= 50 V \end{aligned}$$

$$\begin{aligned} R_4 &= 5 k\Omega \\ R_5 &= 6 k\Omega \\ R_7 &= 7 k\Omega \\ R_6 &= 1 k\Omega \end{aligned}$$

$$R_e = \left((R_1 + R_2) \times R_4 \right) + \left(R_3 + R_5 \right) + R_6 \times R_7 = 3,2 k\Omega \Rightarrow I = U / R_e = 50 V / 3,2 k\Omega = \underline{15,625 mA}$$

$\underbrace{5 k\Omega \quad 2,5 k\Omega}_{2,5 k\Omega} \quad \underbrace{4 k\Omega \quad 2,4 k\Omega}_{2,4 k\Omega} \quad \underbrace{2,5 k\Omega \quad 2,4 k\Omega}_{5,9 k\Omega}$

$$U = U_{R7} = 50 V$$


$$I_{R7} = U_{R7} / R_7 = 50 V / 7 k\Omega = 7,14 mA \Rightarrow I_{R6} = I - I_{R7} = 15,625 mA - 7,14 mA = \underline{8,485 mA}$$

$$U_{R4} = U_{R1} + U_{R2}$$

$$U_{R3} = U_{R5}$$

$$U_{R6} + U_{R4} + U_{R5} = U$$

egyszerűsített ábra

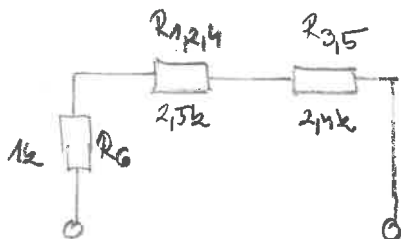

$$U_{R6} = U \cdot \frac{R_6}{R_{\Sigma}} = \underline{8,42 V}$$

$$U_{R1,2,4} = U \cdot \frac{R_{1,2,4}}{R_{\Sigma}} = \underline{21,18 V}$$

$$U_{R3,5} = U \cdot \frac{R_{3,5}}{R_{\Sigma}} = \underline{20,33 V}$$

$$I_{R3} = U_{R3,5} / R_3 = 20,33 V / 4 k\Omega = \underline{5,08 mA}$$


$$I_{R5} = U_{R3,5} / R_5 = 20,33 V / 6 k\Omega = \underline{3,388 mA}$$

$$\sum I_{R3} + I_{R5} = I_{R6}$$

$$I_{R4} = U_{R1,2,3} / R_4 = 21,18V / 5k\Omega = 4,236mA$$

$$I_{R1,2} = I_{R4} = 4,236mA$$
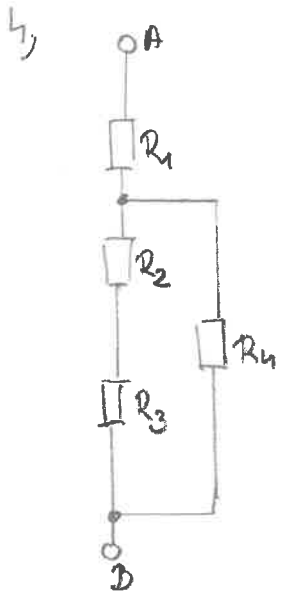
$$\left. \begin{aligned} U_{R1} &= I_{R1,2} \cdot R_1 = 4,236mA \cdot 2k\Omega = 8,472V \\ U_{R2} &= I_{R1,2} \cdot R_2 = 4,236mA \cdot 3k\Omega = 12,708V \end{aligned} \right\} U_{R1} + U_{R2} = U_{R1,2,3}$$



$$U_{AB} = 14V$$

$$R_1 = 1k\Omega$$


$$R_2 = 4,7k\Omega$$

$$R_3 = 800\Omega$$

$$R_4 = 98k\Omega$$

$$U_{R4} = U \cdot \frac{(R_2 + R_3) \times R_4}{((R_2 + R_3) \times R_4) + R_1} = 10,54V$$
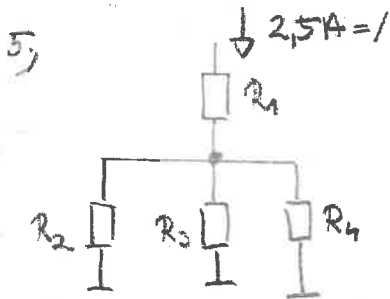
$$\left. \begin{aligned} U_{R3} &= U_{R4} \cdot \frac{R_3}{R_2 + R_3} = 1,63V \\ U_{R2} &= U_{R4} \cdot \frac{R_2}{R_2 + R_3} = 8,91V \end{aligned} \right\} U_{R2} + U_{R3} = U_{R4}$$




$$R_1 = 800\Omega$$

$$R_2 = 1k\Omega$$

$$R_3 = 4,7k\Omega$$

$$R_4 = 960\Omega$$
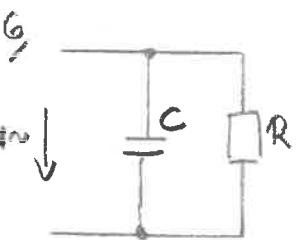
$$\left. \begin{aligned} I_{R2} &= I \cdot \frac{R_3 \times R_4}{R_2 + (R_3 \times R_4)} = 1,1A \\ I_{R3} &= I \cdot \frac{R_2 \times R_4}{R_3 + (R_2 \times R_4)} \approx 0,236A \\ I_{R4} &= I \cdot \frac{R_2 \times R_3}{R_4 + (R_2 \times R_3)} = 1,15A \end{aligned} \right\} \frac{I_{R1} + I_{R2} + I_{R3}}{1} = 2,5A$$



$$U = 5V$$

$$C = 100nF$$

$$R = 1,5k\Omega$$

$$f = 1k\text{Hz}$$

$$a) X_C = \frac{1}{2\pi f C} = 1,59k\Omega$$

$$I_R = U / R = 3,33mA$$

$$I_C = U / X_C = 3,14mA$$

$$I^2 = I_R^2 + I_C^2 \Rightarrow I = \sqrt{I_R^2 + I_C^2} = 4,57mA$$

$$b) Z = \frac{U}{I} = \frac{5V}{4,57mA} = 1,09k\Omega$$

$$Z = \frac{1}{\sqrt{(1/R^2) + (1/X_C^2)}} = 1,09k\Omega$$

$$a) I, I_R, I_C$$


$$b) Z$$

$$c) \varphi + \text{vector}$$



tapirum tapirszállítás

2025#


g) vektoralgebra

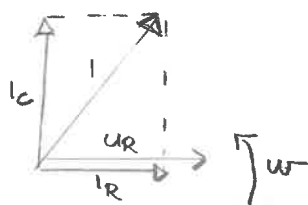

- VAGY -

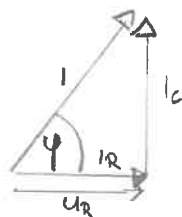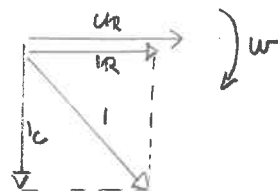
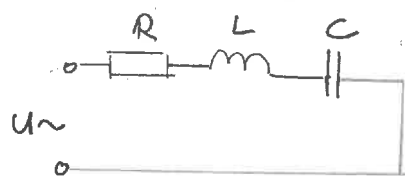
$$\varphi = \tan^{-1} \frac{I_C}{I_R} = 40,0^\circ$$



$$U = 6V$$

$$X_L = 2,5k\Omega$$

$$X_C = 4k\Omega$$

$$f = 5kHz$$

$$R = 2k\Omega$$

- a) Z_i
b) U_R, U_C, U_L
c) L, C

$$a) Z = \sqrt{R^2 + (X_L - X_C)^2} = 2,5k\Omega$$

$$I = U/Z = 6V/2,5k\Omega = 2,4mA$$

$$b) U_R = I \cdot R = 2,4mA \cdot 2k\Omega = 4,8V$$

$$U_C = I \cdot X_C = 2,4mA \cdot 4k\Omega = 9,6V$$


$$U_L = I \cdot X_L = 2,4mA \cdot 2,5k\Omega = 6V$$

$$\sum U = U$$

$$U = \sqrt{U_R^2 + (U_C - U_L)^2} = U$$

$$c) X_L = 2\pi f L \Rightarrow L = \frac{X_L}{2\pi f} = \frac{2,5k\Omega}{2\pi \cdot 5kHz} = 79,6mH$$
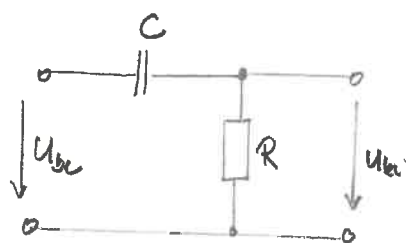
$$X_C = \frac{1}{2\pi f C} \Rightarrow C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi \cdot 5kHz \cdot 4k\Omega} = 7,96nF$$



$$U_{be} = 15V$$

$$f = 2,5kHz$$

$$R = 20,2k\Omega$$

$$a) C \text{ i } h_a \text{ f } 3,2kHz$$

$$b) Z_{be} \text{ i } h_{be} (@ 2,5kHz)$$

$$c) U_{ki} \text{ i } \varphi$$

d) A kimenetett egy $4,71k\Omega$ -os ellenállással terhelhető. Adja meg az ω határfrekvenciát!


$$a) \left. \begin{array}{l} R = X_C \\ R = \frac{1}{2\pi f C} \end{array} \right\} \Rightarrow C = \frac{1}{2\pi R \cdot f_h} = \frac{1}{2\pi \cdot 20,2k\Omega \cdot 3,2kHz} = 15nF$$

$$b) X_C = \frac{1}{2\pi \cdot f \cdot C} = \frac{1}{2\pi \cdot 45 \text{ kHz} \cdot 15 \text{ nF}} = \underline{4,24 \text{ k}\Omega}$$

$$Z_{bc} = \sqrt{R^2 + X_C^2} = \sqrt{3,3^2 \text{ k}\Omega + 4,24^2 \text{ k}\Omega} = \underline{5,37 \text{ k}\Omega}$$

$$I_{bc} = U_{bc} / Z_{bc} = 15 \text{ V} / 5,37 \text{ k}\Omega = \underline{2,79 \text{ mA}}$$
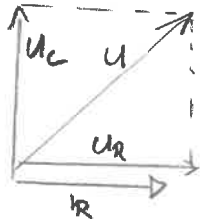
$$c) U_{bc} = U_{bc} \cdot \frac{R}{Z} = 15 \text{ V} \cdot \frac{3,3 \text{ k}\Omega}{5,37 \text{ k}\Omega} = \underline{9,21 \text{ V}}$$



ϕ

$$\phi = \tan^{-1} \frac{U_C}{U_R} = \tan^{-1} \frac{X_C}{R} = 52,1^\circ$$