



## Experiment No. 6

### Audio Tone Control Amplifier

**By:** Prof. Gabriel M. Rebeiz  
The University of Michigan  
EECS Dept.  
Ann Arbor, Michigan

#### Purpose


To build and test a tone control amplifier and to study the effect of the capacitor on the corner frequency of an RC circuit.

- Read this experiment and answer the pre-lab questions before you come to the lab.

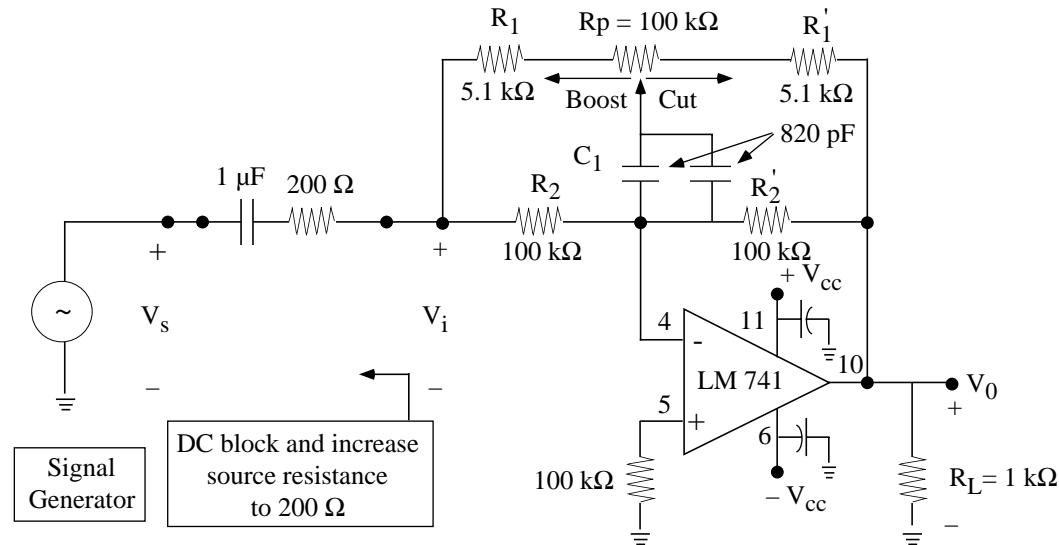
#### 6.1 Treble Tone Control Amplifier:

**Equipment:** The whole Agilent rack.

A treble tone control amplifier is shown below:



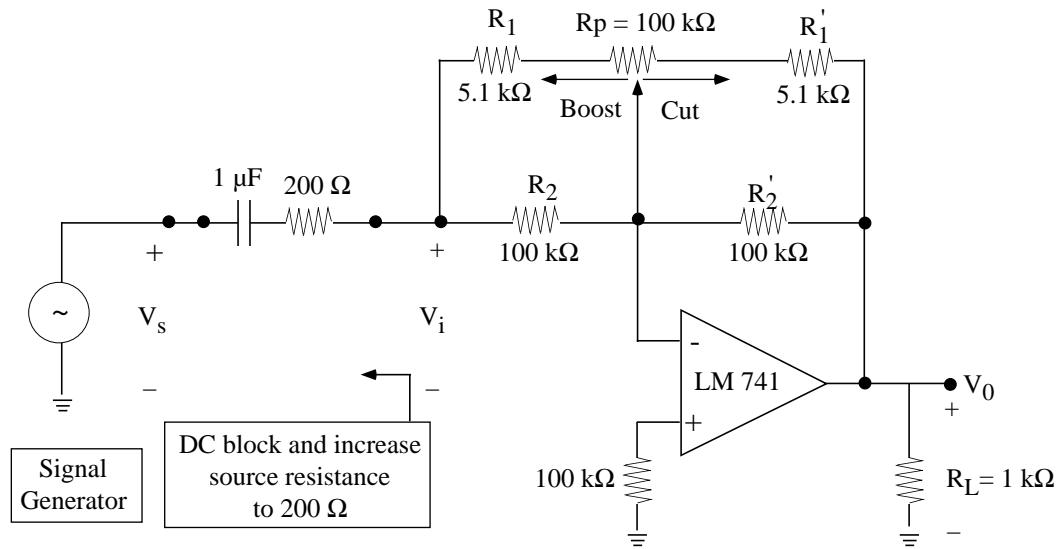At high frequencies, when the  $C_1$  ( $2 \times 820\ pF$ ) behaves as a short-circuit, the circuit becomes:



If the 100 kΩ potentiometer is set at maximum boost, the gain becomes:


$$\frac{V_0}{V_i} = -\frac{R'_2 \parallel (R_p + R'_1)}{R_2 \parallel R_1} \approx 10.5 \text{ (20.4 dB) at high frequencies.}$$

If the 100 kΩ potentiometer is set at maximum cut, the gain becomes:

$$\frac{V_0}{V_i} = -\frac{R'_2 \parallel R'_1}{R_2 \parallel (R_p + R_1)} \approx 0.095 \text{ (-20.5 dB) at high frequencies.}$$

At any frequency, if the 100 kΩ potentiometer is set exactly in the middle, the circuit is perfectly symmetrical and no current passes by C1 (whatever its value). The capacitor C1 can therefore be removed from the circuit, and the gain becomes  $\frac{V_0}{V_i} = \frac{-R'_2}{R_2} = -1 \text{ (0 dB)}$ ,

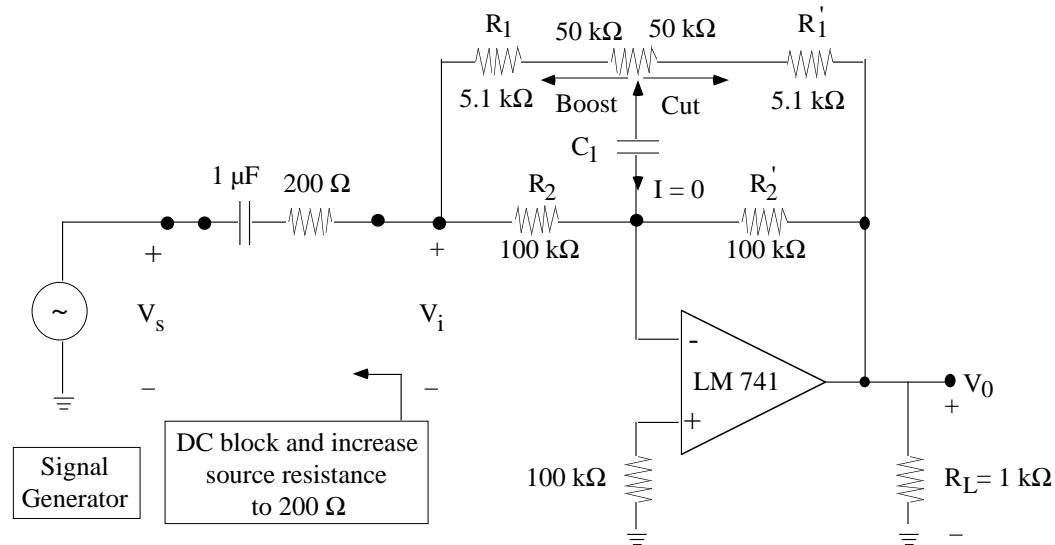which is the flat response over the entire frequency range.




The corner frequency, defined for max. boost/cut positions, is where the transfer function deviates from the flat response by  $\pm 3$  dB. It is given by:

$$f_H = \pm 3\text{-dB frequency} = \frac{1}{2\pi R_2 C_1}$$

$$f_H \sim 1.0 \text{ kHz for } C_1 = 2 \times 820 \text{ pF, } R_2 = 100 \text{ k}\Omega$$

$$f_H \sim 2.0 \text{ kHz for } C_1 = 820 \text{ pF, } R_2 = 100 \text{ k}\Omega$$

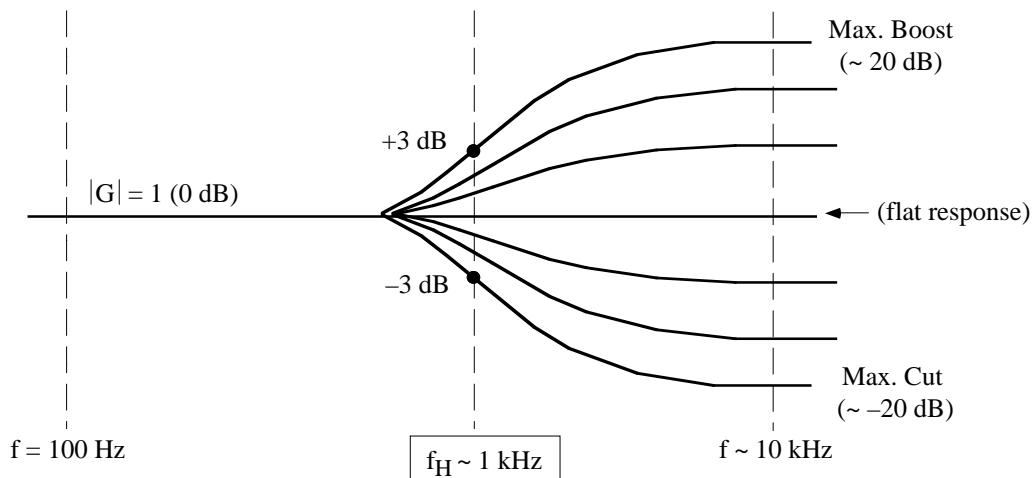The transfer function for the treble control amplifier and  $C_1 = 2 \times 820 \text{ pF}$  "looks" like:



1.  Draw the circuit in your notebook.
2. Assemble the circuit on the breadboard. Do not forget to connect two  $200 \mu\text{F}$  capacitors from  $+V_{cc}$  (+12 V) to ground and from  $-V_{cc}$  (-12 V) to ground for noise

cancellation. Show the T.A. your completed circuit before connecting it to the Agilent power supply.

3. Check the DC voltages at  $V^-$ ,  $V^+$  and  $V_0$  terminals. They should be in the mV level.
4. Set the Agilent 33120A function generator to 400 mV ppk with a frequency of 20 kHz and connect it to the amplifier.

Connect  $V_0$  to channel 1 and  $V_S$  to channel 2 of the scope.

5.  Vary the 100 k $\Omega$  potentiometer and measure  $V_0/V_S$ . Make sure that you have a gain around  $\pm 20$  dB at 20 kHz. Find the position of the potentiometer which results in a gain of 0 dB (gain = -1) at 20 kHz.
6.  Measure the frequency response (amplitude and phase) from 50 Hz–100 kHz (50, 100, 200, ... Hz) at the three gain settings shown below:

#### Phase Measurement:

Remember, you need to do this measurement in time domain so as to measure the time delay and hence the phase. To measure the phase delay between the input and output signals, display both signals on the screen and measure the time difference ( $\Delta t$ ) between the signals. As mentioned in class,  $\text{phase} = (\omega)t = (2\pi f)t$ . Therefore, the phase delay between the input and output signals is  $\Delta\phi = (\omega)\Delta t$ .

Alternatively, you can use the phase delay setting softkey (phase 1-2) under the measure  menu.

#### Gain Settings:

- Maximum Boost ( $|G| \approx 10$ ) – Use  $V_S = 400$  mV ppk
- Maximum cut ( $|G| \approx 0.1$ ) – Use  $V_S = 1$  V ppk
- Flat response ( $|G| \approx 1$ ) (just take few points only). Use  $V_S = 1$  V ppk.

For the max. boost/cut positions, calculate the 3-dB corner frequency ( $f_H$ ) from the measured data.

7.  Remove one of the 820 pF capacitors ( $C_1 = 820$  pF now) and repeat 6 for maximum boost setting (amplitude only). What do you notice? Comment.
8.  Put the 820 pF capacitor back into the circuit,  $C_1 = 2 \times 820$  pF ( $f_H \sim 1$  kHz), set the Agilent 33120A function generator to deliver an 800 Hz square-wave with  $V_{ppk} = 600$  mV. Measure the input waveform ( $V_S$ ) in frequency domain and note the fundamental and harmonic values (up to 13  $f_0$  – 7 measurement points).

Note: Do not measure any even harmonics. These are aliases and you need to check your scope FFT settings.

9.  Connect the function generator to the treble circuit. Measure and sketch accurately the output voltage ( $V_0$ ) in time domain and frequency domain (up to 13  $f_0$ ) for the maximum boost/cut settings. (Make sure that you are not clipping or driving the scope into saturation.).


Comment on your measurements.



## 6.2 Bass Tone-Control Amplifier:

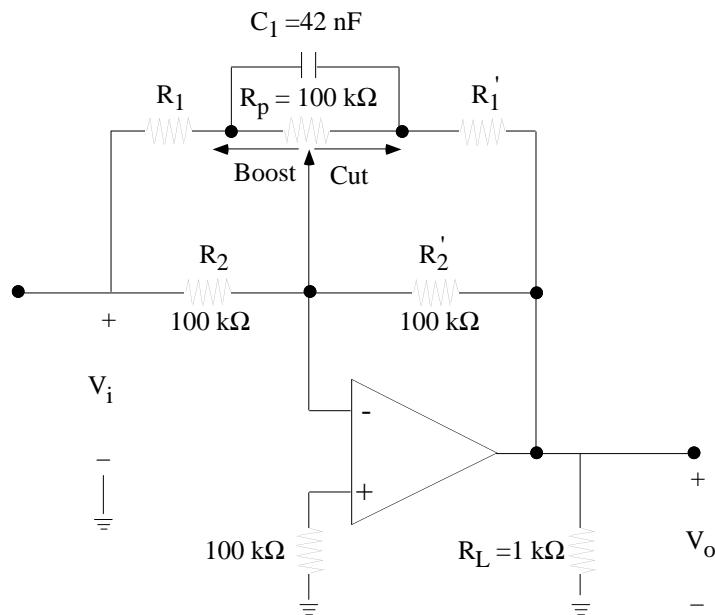**DO NOT BUILD THIS CIRCUIT. I AM INCLUDING IT HERE FOR COMPLETENESS.**

A bass tone control amplifier is shown below:



$$- \text{Max. boost} = \frac{R'_2 \parallel (R_p + R'_1)}{R_2 \parallel R_1} = 10.5$$

*f is very low*

*(capacitor is open-circuited)*

$$- \text{Max. Cut} = \frac{R'_2 \parallel R'_1}{R_2 \parallel (R_p + R_1)} = 0.095$$

*f is very low*

*(capacitor is open-circuited)*

$$- \text{Corner frequency at max. boost/cut settings: } f_L = \frac{1}{2\pi R_1 C_1} \\ = 750 \text{ Hz}$$


$$R_1 = 5.1 \text{ k}\Omega$$

$$C_1 = 42 \text{ nF}$$

– If the potentiometer is set exactly in the middle, then no current passes by  $C_1$  (whatever its value) and we get a flat response ( $|G| \approx 1$ ) over the entire frequency range.



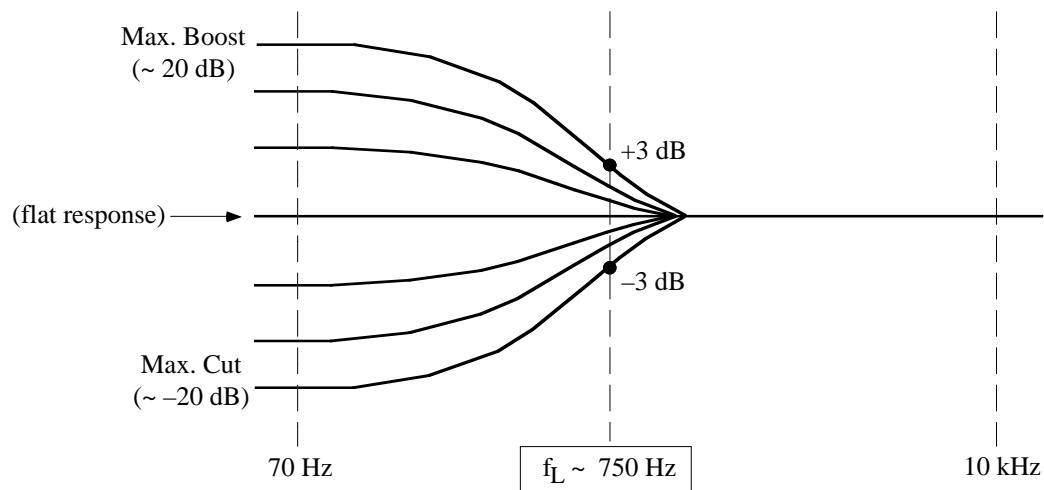The transfer function for the bass control amplifier and  $C_1 = 42 \text{ nF}$  "looks" like:



## Experiment No. 6.


### Audio Tone Control Amplifier

#### Pre-Lab Assignment

- Derive  $V_0/V_i$  (not  $V_0/V_s$ ) for the treble control amplifier at max. boost/cut settings and high frequencies ( $> 20 \text{ kHz}$ , capacitor is short-circuited). The answer is given in the lab assignment.

Derive now  $V_i/V_s$  and  $V_0/V_s$ , paying attention to the input impedance of the amplifier at the max. boost/cut positions and very high frequencies (capacitor is short-circuited).

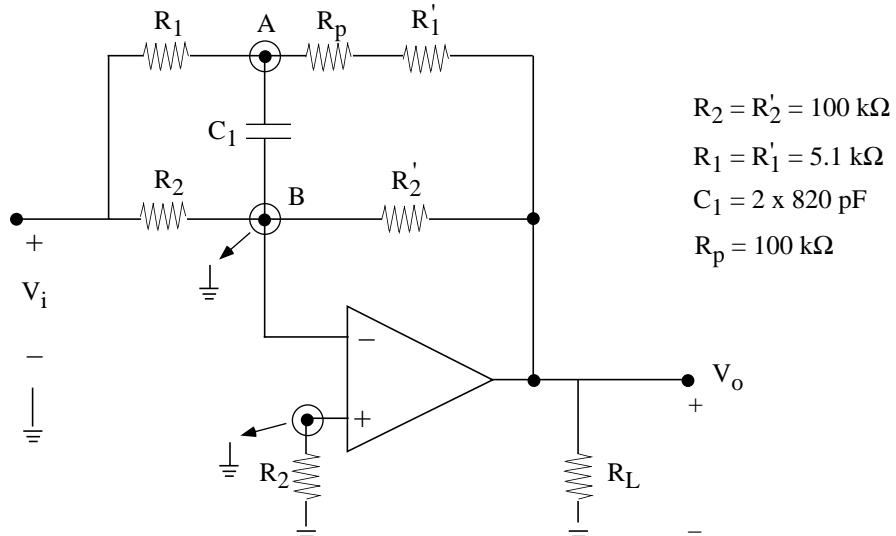- The circuit at maximum boost setting is shown below. Using nodal analysis at nodes A, B, determine the transfer function  $\frac{V_o}{V_i}(\omega)$ .



Note, in order to get a simple and elegant answer, you should make some "accurate" assumptions (to within a few percent):

$$R_p + R'_1 \approx R_p \text{ since } R_p \gg R'_1$$

$$R_1 \parallel R_2 \approx R_1 \text{ since } R_2 \gg R_1$$

$$R'_2 \parallel (R_p + R'_1) \approx \frac{R'_2}{2} \text{ since } R'_2 \approx R_p + R'_1$$

$$\frac{V_o}{V_i}(\omega)$$

a. Put the transfer function  $\frac{V_o}{V_i}(\omega)$  in the form:

$$\frac{V_o}{V_i}(\omega) = H(\omega) = (A) \frac{1+j(\omega/\omega_1)}{1+j(\omega/\omega_2)}$$

$A, \omega_1, \omega_2$  = constants to be determined

$\omega_1$  = zero of transfer function

$\omega_2$  = pole of transfer function

b. Derive  $|H(\omega)|$ , the magnitude of  $H(\omega)$ .

c. Derive the phase of  $H(\omega)$ .

d. Using the component values given above, plot  $(H(\omega))$  on a Bode-plot (dB,  $\log f$ ) from 100 Hz to 100 KHz (dB: -10 to +30).


e. Also, plot the phase of  $H(\omega)$  over the same frequency range.

## Experiment No. 6.

### Audio Tone Control Amplifier

#### Lab Report Assignment

1. Plot the Bode plots (amplitude and phase) ( $V_o/V_s$ ) from 50 Hz - 100 kHz for  $C_1 = 2 \times 820 \text{ pF}$  and the 3 measured treble settings ( $|G| = 10$ ,  $|G| = 0.1$ ,  $|G| = 1$ ) on the same ( $\log f$ , dB) Bode-plot and the same ( $\log f$ , degrees) phase graph. For each case, determine the 3-dB corner frequency. (Use the subplot command in MATLAB to get two plots vertically on the same page).
2. Plot the transfer function ( $V_o/V_s$ ) for max. boost setting (only) from 50 Hz - 100 kHz for  $C_1 = 820 \text{ pF}$  and  $C_1 = 2 \times 820 \text{ pF}$  on the same  $\log f$ , dB graph (amplitude only). Comment on the 3-dB corner frequency of each case.
3. The tone control amplifier can be represented as a block diagram with a transfer function,  $H(\omega)$  in frequency domain.

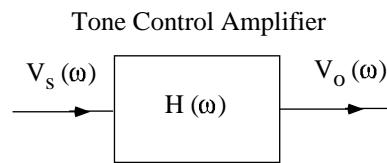

$$\frac{V_o}{V_s}(\omega) = H(\omega)$$

$$V_o(\omega) = H(\omega) \cdot V_s(\omega)$$

$$\text{Amplitude: } V_o/\text{dB} = H(\omega)/\text{dB} + V_s/\text{dB}$$

$$\text{Phase: } \angle V_o = \angle H(\omega) + \angle V_s$$

$V_s(\omega)$  = Input signal (in frequency domain).

$H(\omega)$  = Measured transfer function of the treble control circuit (in frequency domain, dB and degrees).

$V_o(\omega)$  = Output signal (in frequency domain).

- 3.1 Calculate the input spectrum (up to  $13f_0$ -amplitude and phase) of an 800 Hz square wave with  $V_{ppk} = 600 \text{ mV}_{ppk}$  (you know how to calculate this using Fourier Series).
- 3.2 Using the measured transfer function  $H(\omega)$  and the spectrum of  $V_i$  (calculated in 3.1), calculate the output spectrum (up to  $13f_0$  – amplitude and phase) at max. boost/cut settings.
- 3.3 Compare the calculated output spectrum (up to  $13f_0$ -amplitude only) for max. boost/cut positions with the measured values in the lab.
- 3.4 This part should be done in MATLAB:

Knowing the amplitude/phase information of  $V_o(\omega)$  (calculated in 3.2), and using Mat-Lab for the sine-wave addition, calculate  $V_o(t)$  for the max. boost/cut positions. (Do not ignore the phase, it is very important!). Compare your results with the time-domain measurements of  $V_o(t)$  done in the lab.

Explain why at max. boost there are sharp peaks in the output waveform, and why at max. cut, there are slow rising edges in the output waveform.

NOTE: This is really not hard. You have some similar sine-wave additions in Lab #2.




## Experiment No. 6.

### Audio Tone Control Amplifier

#### Worksheet/Notes

##### Treble Control Amplifier

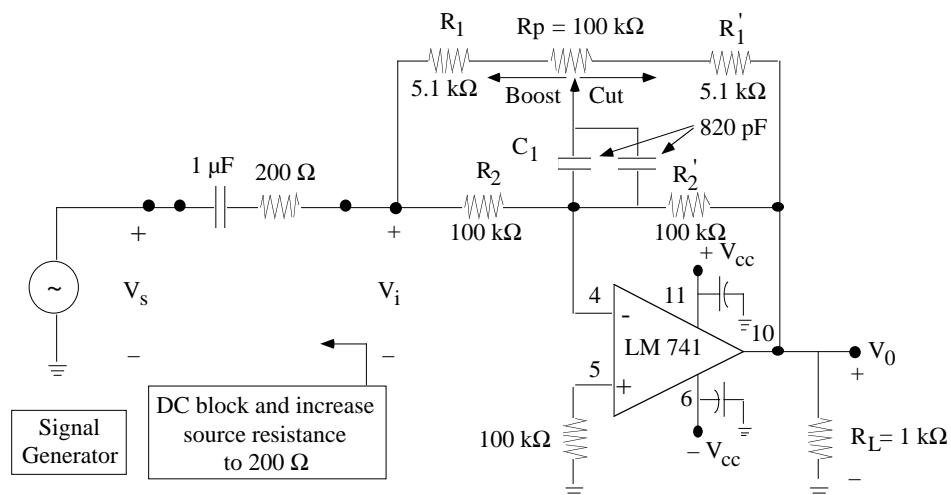




## Experiment No. 6.

### Audio Tone Control Amplifier

#### Worksheet/Notes


##### Bass Control Amplifier

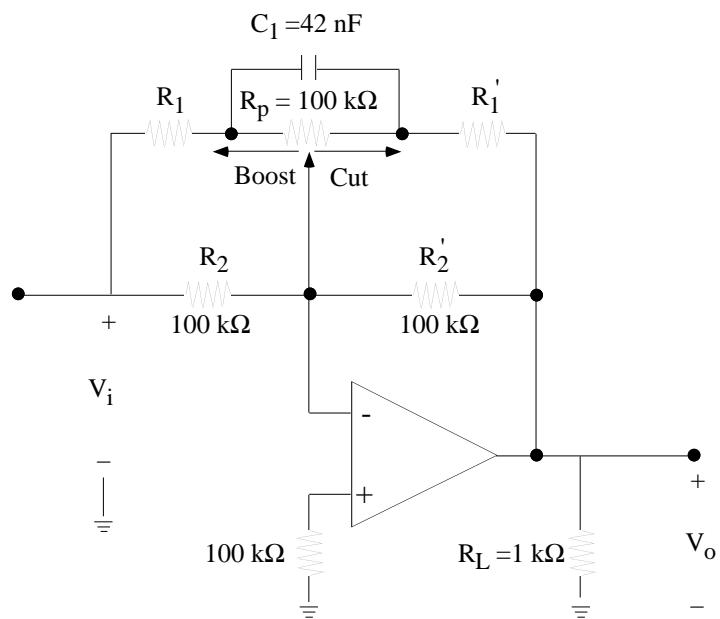


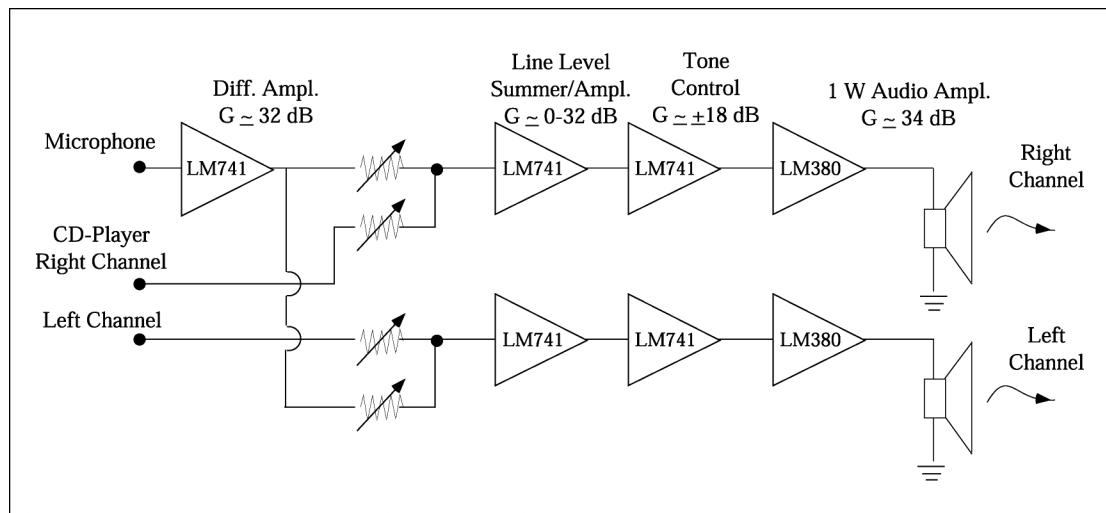
### Open Audio Lab

You are welcome to show up in the lab and test a complete audio amplifier assembled from the components which you built and tested during the term. You can talk into a microphone or use a CD-input. The output will be in stereo mode. BRING YOUR FAVORITE CD and listen to it, mix your voice with music and create weird sound effects. The audio system is:




^^ Enjoy ^^



## Appendix A

### Color Coding of Resistors/Capacitors

Color	Significant Figure	Decimal Multiplier ( $10^*$ )
Black	0	1
Brown	1	10
Red	2	100
Orange	3	1,000
Yellow	4	10,000
Green	5	100,000
Blue	6	1,000,000
Violet	7	10,000,000
Gray	8	100,000,000
White	9	1,000,000,000
Gold	—	0.1
Silver	—	0.01
No Color	—	—

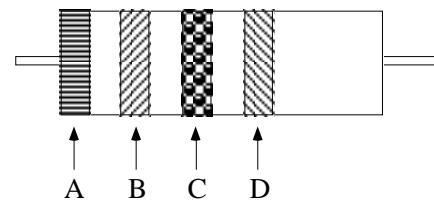

$$R = AB \times 10^C \%D$$

Standard Resistance Values	
1.0, 1.2, 1.5, 1.8, 2.0, 2.2, 2.4, 2.7, 3, 3.3, 3.6, 3.9, 4.3, 4.7, 5.1., 5.6, 6.2, 6.8, 7.5, 8.2, 9.1	

Axial Leads	Color
A	Indicates first significant figure of resistance value in ohms.
B	Indicates second significant figure.
C	Indicates decimal multiplier.
D	If any, indicates tolerance in percent about nominal resistance value. If no color appears in this position, tolerance is 20%.

<b>Examples:</b>	$R = 2.2 \text{ k}\Omega$	Red, Red, Red	$(22 \times 10^2)$
	$R = 1.0 \text{ k}\Omega$	Brown, Black, Red	$(10 \times 10^2)$
	$R = 100 \text{ k}\Omega$	Brown, Black, Yellow	$(10 \times 10^4)$
	$R = 560 \Omega$	Green, Blue, Brown	$(56 \times 10^1)$
	$R = 47 \Omega$	Yellow, Violet, Black	$(47 \times 10^0)$